

MODEL PAPER – FORMATIVE ASSESSMENT-1
C-23-EE-303
BOARD DIPLOMA EXAMINATION, (C-23)
DEEE – THIRD SEMESTER EXAMINATION
EE-303 :AC circuits & Transformers

Time: 90 Minutes

Total Marks: 40M

PART-A

(1 x 4) + (4 x 3) = 16M

Instructions: Answer all five questions.

First question carries four marks and remaining each question carries three marks.

Answers should be brief and straight to the point and shall not exceed five simple sentences

- 1.(a) If instantaneous voltage $e=100\sin(50t)$, its RMS value is _____. CO1
(b) The polar form of $3-j4$ is _____. CO1
(c) The relation between voltage and current in a pure inductance is _____. CO2
(d) The phase angle between any two phases in a three phase system is 120 degrees. True / False. CO3
2. Define (a) frequency (b) Form Factor related to A.C. quantity. CO1
3. A sinusoidal current wave is given by $i= 100\sin 100 \pi t$.Determine (i) Average value and (ii) R.M.S value CO1
4. Define resonance of a RLC series circuit. CO2
5. List any three advantages of 3-phase system over single phase system. CO3

PART-B

3X8=24 MARKS

Instructions: Answer all three questions.

Each question carries eight marks.

The answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.

- 6.(a)Derive the Average value, RMS value and form factor of a fullwave rectified sinewave. CO1
(OR)
(b) Perform the following where $A=6+j8, B=8-j10$ CO1
(i) $A+B$ (ii) $A-B$ (iii) AXB (iv) $A \div B$
- 7.(a) A coil of resistance 6Ω and an inductance of 0.03 H is connected across of 50 V , 60 Hz supply. Find the (i) current, (ii) phase angle, (iii) power factor and (iv) power. CO2
(OR)
(b) A resistance of 50Ω , inductance of 100mH and a capacitance of $100\mu\text{F}$ are connected in series across 200V , 50Hz supply. Determine (i) Impedance (ii) current flowing through the circuit (iii) power factor (iv) power in watts. CO2
- 8.(a) Each phase of delta connected load comprises a resistor of 60Ω and capacitance of $40\mu\text{F}$ in series. Calculate line and phase currents, total power when the load is connected to a 440V , 3-phase, 50Hz supply. CO3
(OR)
(b)) Derive the equation for power and power factor of a three-phase balanced load using two-wattmeter method. CO3

MODEL PAPER – FORMATIVE ASSESSMENT-2
C-23-EE-303
BOARD DIPLOMA EXAMINATION, (C-23)
DEEE – THIRD SEMESTER EXAMINATION
EE-303 :AC circuits & Transformers

Time: 90 Minutes

Total Marks: 40M

PART-A

(1 x 4) + (4 x 3) = 16M

Instructions: Answer all five questions.

First question carries four marks and remaining each question carries three marks.

Answers should be brief and straight to the point and shall not exceed five simple sentences

- 1.(a) For step down Transformers, the transformation ratio is less than 1 : (True / False) CO4
(b) The condition for maximum efficiency of Transformer is _____. CO4
(c) Any one advantage of autotransformer is _____. CO5
(d) Any one method of cooling of power transformer is _____. CO5
2. Define all-day efficiency of a transformer. CO4
3. Distinguish between shell-type and core-type transformers in any three aspects. CO4
4. State the advantages of 3-phase transformer over single phase transformer. CO5
5. List the special transformers. CO5

PART-B

3X8=24 MARKS

Instructions: Answer all three questions.

Each question carries eight marks.

The answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.

- 6.(a) Explain the working principle of transformer. CO4
(OR)
(b) Derive the EMF equation of a single-phase transformer. CO4
- 7.(a) Draw the equivalent circuit diagram refers to primary for a 4 kVA, 200/400 V and 50 HZ 1 – ϕ transformer from the test results as follows:
OC Test : 200 V, 0.8 A, 80 W on LV Side
SC Test : 20 V, 10 A, 100 W on HV Side CO4
(OR)
(b) Draw the Vector diagram of a practical transformer on load for unity power factor and lagging power factor. CO4
- 8.(a)State the need for parallel operation of three phase transformers and also state the conditions for parallel operation of three phase transformers. CO5
(OR)
(b))Explain the function of each part in a power transformer. CO5

MODEL PAPER – SUMMATIVE EXAMINATION
C-23-EE-303
BOARD DIPLOMA EXAMINATION, (C-23)
DEEE – THIRD SEMESTER EXAMINATION
EE-303 : AC circuits & Transformers

Time: 3 hours

Total marks: 80

PART-A

10 X 3 = 30

Instructions:

- i. Answer all questions.
- ii. Each question carries three marks.
- iii. Answers should be brief and straight to the point and shall not exceed five simple sentences

1. State the relation between number of poles, speed and frequency CO1
2. Define the terms related to A.C. quantity (i) RMS value and (ii) peak factor. CO1
3. The given two vectors are $A=30+j52$ and $B= 30-j52$. Perform the functions. CO1
(i) $A+B$ (ii) $A \times B$
4. Define resonance of series circuit and state the formula for resonance frequency. CO2
5. A resistance of 4Ω is connected in series with an inductance of $0.02H$ across the supply of $200V, 50Hz$.
Find current in the circuit. CO2
6. List any three advantages of 3-phase system over single phase system. CO3
7. State the concept of phase sequence. CO3
8. Classify the transformers based on number of phases. CO4
9. Define all-day efficiency of a transformer. CO4
10. List the special transformers CO5

PART-B

5 X 10 =50M

Instructions:

- i. Answer any five questions.
- ii. Each question carries ten marks.
- iii. The answers should be comprehensive and the criteria for valuation are the content but not the length of the answer.

11. Derive an expression for impedance, current, phase angle, power and power factor of an AC

- circuit consisting of resistance and a pure capacitor in series. CO2
12. A resistance of 50Ω , inductance of 100 mH and a capacitance of $100\ \mu\text{F}$ are connected in series across 200V, 50Hz supply. Determine
 (i) Impedance (ii) current flowing through the circuit (iii) power factor
 (iv) power in watts. CO2
13. Derive the equation for power and power factor of a three-phase balanced load using two-wattmeter method. CO3
14. Each phase of delta connected load comprises a resistor of 60Ω and capacitance of $40\ \mu\text{F}$ in series. Calculate line and phase currents, total power when the load is connected to a 440V, 3-phase, 50Hz supply. CO3
15. Draw the equivalent circuit diagram referred to primary for a 4 kVA, 200/400 V and 50 Hz $1 - \phi$ transformer from the test results as follows:
 OC Test : 200 V, 0.8 A, 80 W on LV Side
 SC Test : 20 V, 10 A, 100 W on HV Side CO4
16. Draw the Vector diagram of a practical transformer on load for unity power factor and lagging power factor. CO4
17. Draw a legible sketch of Power transformer and explain the function of each part. CO5
18. State the necessity of cooling of power transformers and list methods of cooling of power transformers. CO5